

Worksheet Solution

(Chapter 1 Kirchhoff's Law)

MCQ (Multiple Choice Questions)

Ans. 1: (a)

Solution: The sum of the currents entering a node is equal to the sum of the currents leaving the node.

$$\begin{aligned} \therefore I_0 + 10 \text{ A} &= 4 \text{ A} + 2 \text{ A} \\ \Rightarrow I_0 &= -4 \text{ A} \end{aligned}$$

Ans. 2: (b)

Solution: Applying KVL

$$-3 + 4I + 5 + 6I = 0 \Rightarrow 10I = -2, \therefore I = -0.2 \text{ A}$$

Ans. 3: (c)

Solution: Total Resistance in the circuit

$$R_{eq} = R + \frac{10 \times 10}{10 + 10} = R + 5$$

$$I = \frac{V}{R_{eq}} = \frac{100}{R + 5} = 8$$

$$8R + 40 = 100 \Rightarrow R = 7.5 \Omega$$

Ans. 4: (b)

Solution: Let the potential at node a is V

Applying KCL at node a

$$\frac{5 - V}{5} + 1 - \frac{V}{15} = 0$$

$$\frac{15 - 4V}{15} + 1 = 0$$

$$4V - 15 = 15 \Rightarrow V = 7.5 \text{ V}$$


$$I = \frac{V}{15} = \frac{7.5}{15} = 0.5 \text{ A}$$

Ans. 5: (b)

Solution: The circuit can be redrawn in the form of voltage source (source transformation technique)

Applying KVL, $-20 \text{ V} + I \cdot 10 \text{ k}\Omega - 8 \text{ V} = 0$

$$I = \frac{28}{10 \text{ k}\Omega} = 2.8 \text{ mA}$$

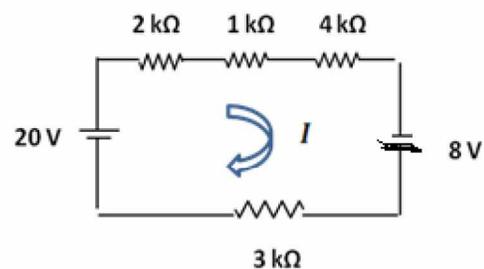

Ans. 6: (a)

Ans. 7: (c)

MSQ (Multiple Select Questions)

Ans. 8: (b), (d)

Solution: Decrease in R_1 leads to a decrease in voltage drop across R_1 , also R_2 and R_3 are parallel so there will be decrease in voltage drop across R_2 which will result in less power dissipated in R_2 . So option b & d are correct